

1. Active passive elements, unilateral bilateral elements, linear non linear elements.
2. KCL, KVL, nodal, mesh, thevenin, norton, superposition, max power transfer
3. Source conversation, star delta conversation
4. Current division & voltage division
5. R,L,C CIRCUIT

DC NETWORKS

- Ohm's Law
- KCL, KVL
- Network Reduction theorem → (Thennings, Norton's)
- Superposition , M.P.T theorem .

Ohms Law :-

According to ohms law the potential difference across any two point of the conductor , will be directly proportional to the current flowing through it.

$$V \propto I$$


$$V = IR$$

KVL :- (mesh analysis)


According to the Kirchoff's voltage law . In any closed circuit or mesh, the algebraic sum of all the emfs and voltage drops will be zero.

Principal of conservation , energy given = energy consumed.
 \therefore net supply voltage = net voltage drop
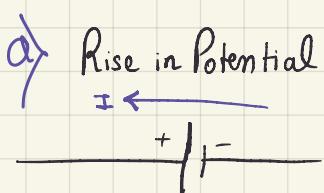
$$\text{Hence } \sum E_{\text{mf}} + \sum IR = 0$$



rise in potential
(+ve)

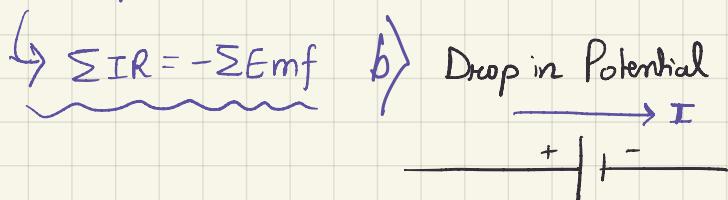


drop in potential (-ve)
potential Drop

KCL :- (nodal analysis)

According to Kirchoff's current law , The algebraic sum of all the currents meeting at a point on a junction will be zero.

$$\sum I = 0$$

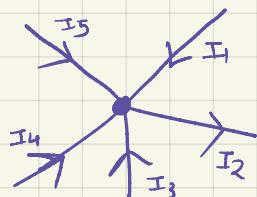


KVL : Mesh Analysis Method

- Difference between mesh & loop

Closed path through which electric current flows. There can't be any other loop/circuit inside it.

There can be various loop inside loop.

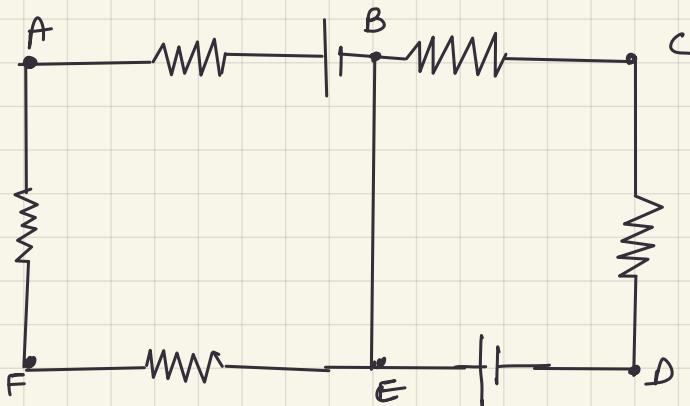

Number of mesh \Rightarrow 2 (ABEF, BCDE)

Number of loop \Rightarrow 3 (including the whole circuit).
(ABEF, BCDE, ACDF)

Type of Questions.


1) Type 1: Voltage sources + Resistance

2) Type 2:- Voltage source + Resistance + Current Source (outer loop).

3) Type 3:- Voltage source + Resistance + Current Source (inner loop)
(shared with 2 mesh).

Type 1 : Voltage, Resistance

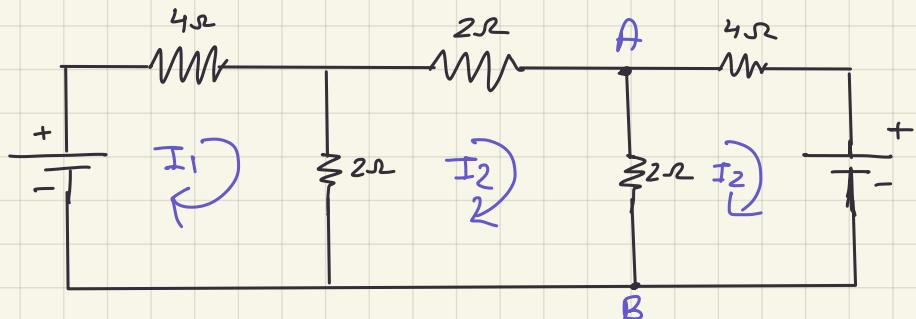- Q1. Calculate the current in branch AB of 2Ω resistor for the given circuit using mesh analysis method.



Soln:-

Step 1:- Identify number of mesh

→ There are 3 mesh.

Step 2:- Decide the direction of loop (current)

→ Clockwise current, I_1, I_2, I_3

Step 3:- Form the equations for each mesh.

→ Here we will get 3 equations,

We Know $\sum Emf + \sum IR = 0$

Applying KVL in mesh ①:-

$$\begin{aligned} & 10 - I_1 \cdot 4 - 4(I_1 - I_2) = 0 \\ \Rightarrow & 10 - 4I_1 - 4I_1 + 4I_2 = 0 \\ \Rightarrow & 10 - 8I_1 + 4I_2 = 0 \quad \text{--- (1)} \end{aligned}$$

Applying KVL in mesh ②:-

$$\begin{aligned} & -4(I_2 - I_1) - 2(I_2) - 2(I_2 - I_3) = 0 \\ \Rightarrow & -8I_2 + 4I_1 - I_3 = 0 \\ \Rightarrow & 4I_1 - 8I_2 - I_3 = 0 \quad \text{--- (2)} \end{aligned}$$

Applying KVL in mesh ③:-

$$\begin{aligned} & -20 - 2(I_3 - I_2) - 4(I_3) = 0 \\ \Rightarrow & 2I_2 - 6I_3 = 20 \quad \text{--- (3)} \end{aligned}$$

* Current of wires between 2 mesh.

⇒ The calculating mesh's current is taken greater always than the other ones.

Solving ① ② ③

$$I_1 = 1.093 A$$

$$I_2 = -0.312 A$$

$$I_3 = -3.437 A$$

- Therefore resultant current in AB is.


$$I_{AB} = I_2 - I_3$$

$$= -0.312 + 3.437$$

$$I_{AB} = 3.125 A$$

Type - 2: Voltage Source + Resistance + Current Sources (outer loop)

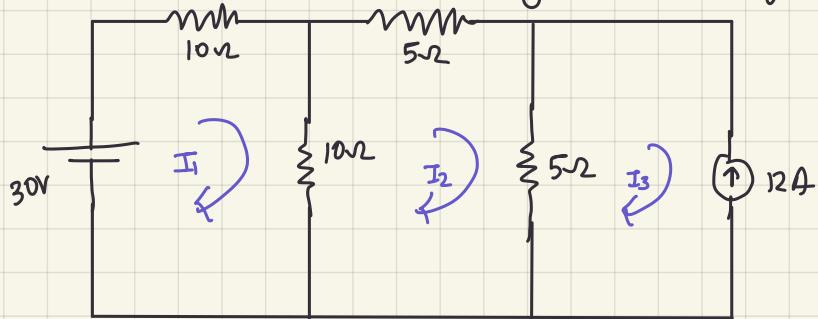Q. Find the current in AB Branch using mesh analysis:-



Soln:- 1) There are 3 meshes

2) I_1, I_2, I_3 in clockwise direction in 3 mesh

3) Forming KVL equation for,

applying KVL in mesh ①

$$\Rightarrow 30 - 10I_1 - 10(I_1 - I_2) = 0$$

$$\Rightarrow 30 - 20I_1 + 10I_2 = 0 \quad \text{--- } ①$$

applying KVL in mesh ②

$$\Rightarrow 10I_1 - 20I_2 + 5I_3 = 0 \quad \text{--- } ②$$

applying KVL in mesh ③

$$\Rightarrow I_3 = -12A$$

(The value of current is already given,
which is opposite to the assumed direction,
so it's negative.)

(3)

Solving ①, ②, ③

$$I_1 = 0A$$


$$I_2 = -3A$$

$$I_3 = -12A$$

\therefore Branch in AB

$$I_{AB} = I_2 = -3A$$

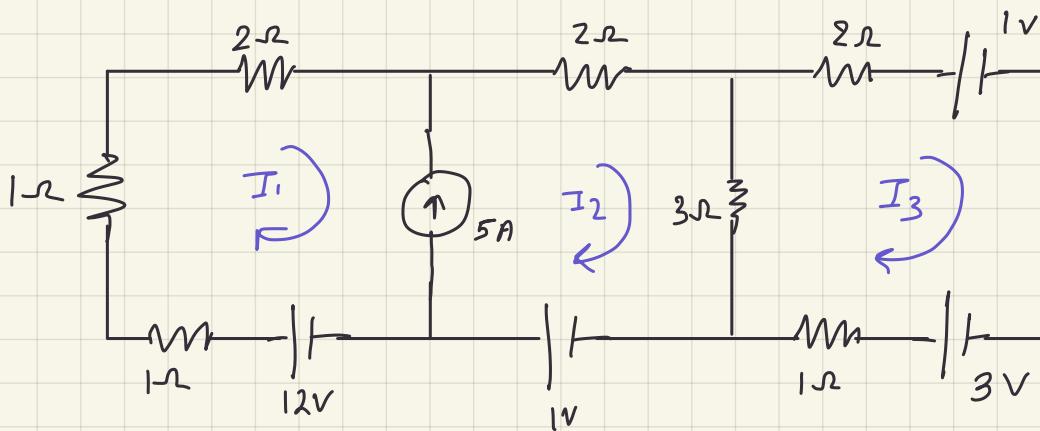
Type - 3: Voltage + Resistance + Current Source (Inside)



Soln:- Supermesh Method

Form eq. of current source first.

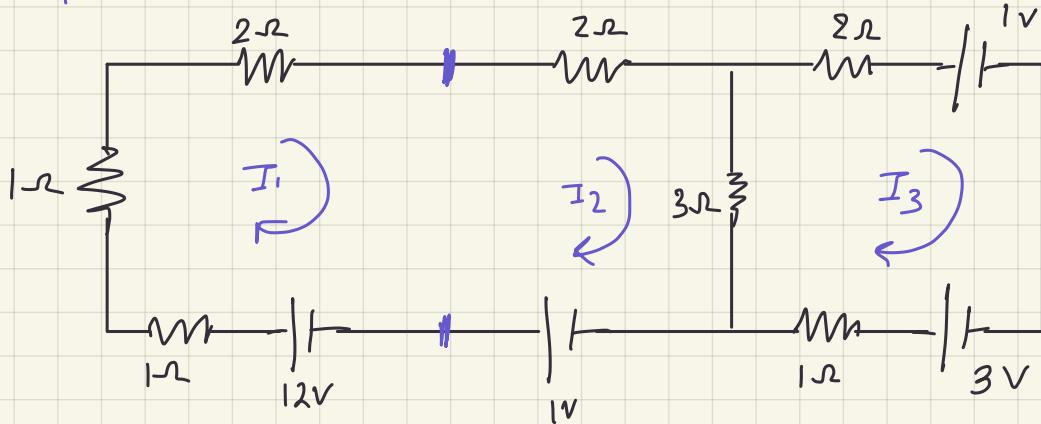- $I_2 - I_1 = 5$ (Since the resultant is in direction of I_2)
(1) $\therefore I_2 > I_1$
- For Supermesh - we can write the combined equation as -



$$\Rightarrow -1I_1 - 1I_1 - 2I_1 - 2I_2 - 3(I_2 - I_3) + 1 + 2 = 0$$

$$\Rightarrow -4I_1 - 5I_2 + 3I_3 + 3 = 0 \quad (2)$$

- Applying KVL in mesh ③

$$0I_1 + 3I_2 - 6I_3 = -2 \quad (3)$$


$$\begin{aligned} \therefore I_1 &= \\ I_2 &= \\ I_3 &= \end{aligned}$$

KCL: Nodal Analysis Method

- Difference between Junction & node

A junction is a point in a circuit where 3 or more than 3 branches combine/divide.

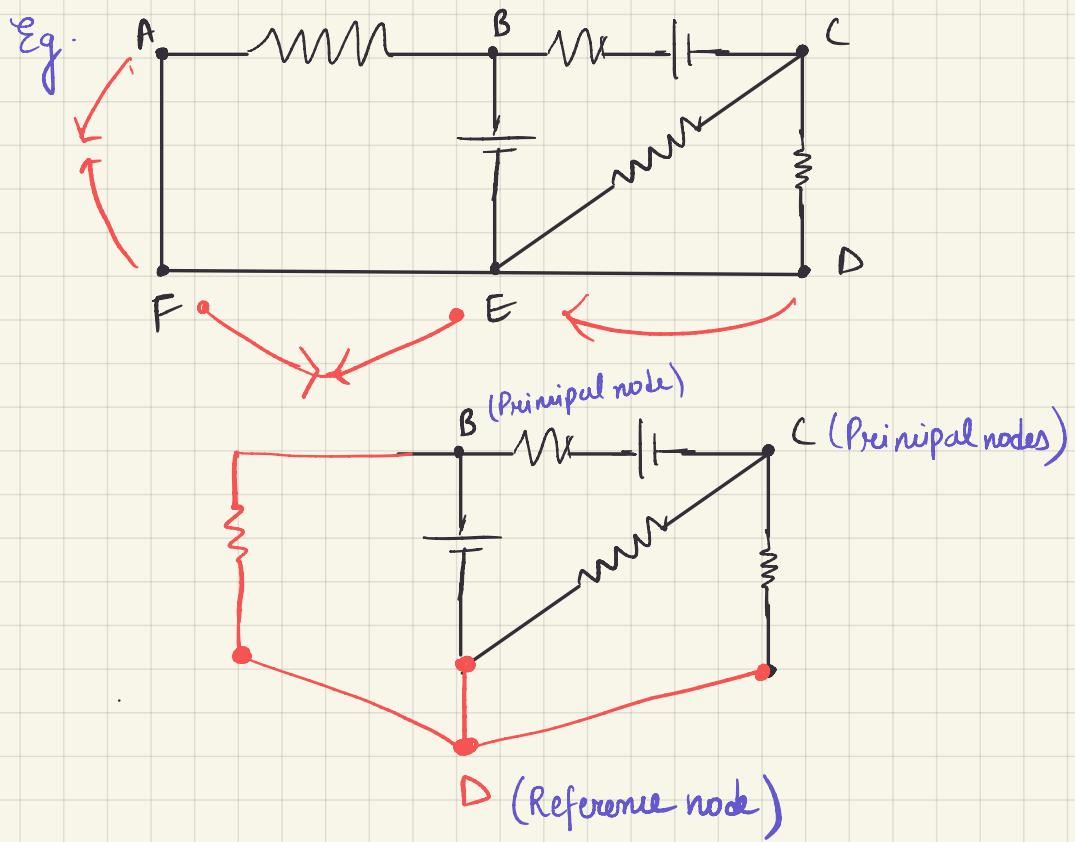It is a point where 2 or more than 2 branches combine (only combine) not divide.




STEPS -

- Identify the principal nodes or junctions present in the network.
- Assign junction potential on each junction with respect to the assigned reference junction having value $V_o = 0V$
- Assuming all the currents in outgoing direction from each junction, form KCL eq.
- Solve the equations to calculate the value of junction potentials.
- Using individual junction potential find the value of required electrical quantity.

Type-1 :- Voltage Source + Resistance

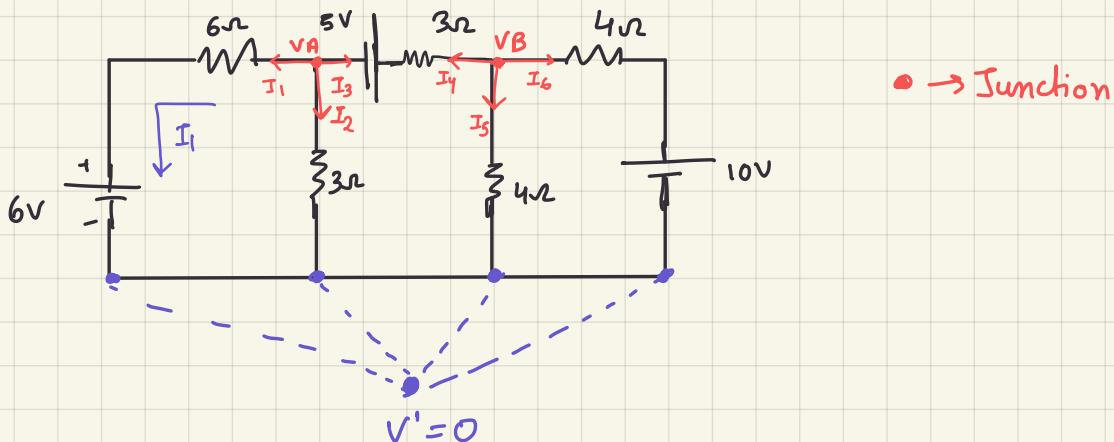Q1. Find the current in 3Ω resistor using KCL.



Soln:- Applying KCL at junction A:-

$$\Rightarrow I_1 + I_2 + I_3 = 0$$

$$\Rightarrow \frac{V_A - V_o - 6}{6} + \frac{V_A - V_o}{3} + \frac{V_A - V_B + 5}{2} = 0$$

$$\Rightarrow \frac{V_A - V_o - 6 + 2V_A - 2V_o + 3V_A - 3V_B + 5}{6} = 0$$

$$\Rightarrow 6V_A - 3V_B = -9 \quad \textcircled{1}$$

Applying KCL in junction 2:-

$$\Rightarrow I_4 + I_5 + I_6 = 0$$

$$\Rightarrow \frac{V_B - V_A - 5}{2} + \frac{V_B - V_o}{4} + \frac{V_B - V_o - 10}{4} = 0$$

$$\Rightarrow 2V_B - 2V_A - 10 + V_B - V_o + V_B - V_o - 10 = 0$$

$$\Rightarrow -2V_A + 4V_B = 20 \quad \textcircled{2}$$

Solving $\textcircled{1}$ & $\textcircled{2}$

$$V_A = 1.333 \text{ V}$$

$$V_B = 5.666 \text{ V}$$


\therefore Current through 3Ω resistor, $\Rightarrow I_2$ current.

$$I_2 = \frac{V_A - V_o}{3} = \frac{V_A}{3} = \frac{1.333}{3}$$

$$I_{(3\Omega)} = 0.444 \text{ A}$$

Type - 2 : Voltage Source + Resistance + Current Source

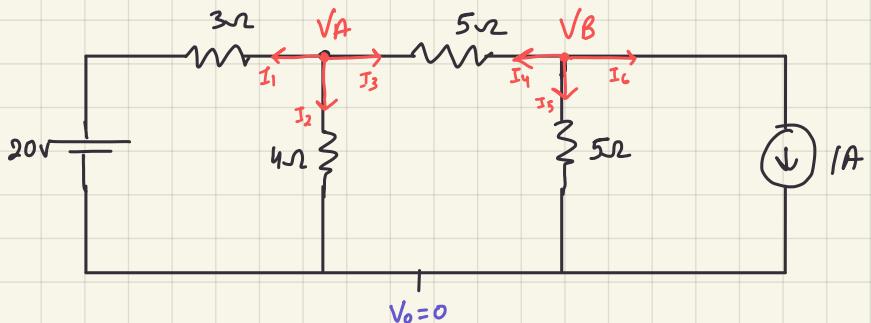Q2. Using nodal analysis find the current in 4Ω branch.



Soln:- Applying KCL at junction A,

$$\begin{aligned} I_1 + I_2 + I_3 &= 0 \\ \Rightarrow \frac{V_A - V_o - 20}{3} + \frac{V_A - V_o}{4} + \frac{V_A - V_B}{5} &= 0 \\ \Rightarrow \frac{20V_A - 400 + 15V_A + 12V_A - 12V_B}{60} &= 0 \\ \Rightarrow 47V_A - 12V_B &= 400 \quad \text{--- (1)} \end{aligned}$$

Applying KCL in junction B,

$$\begin{aligned} \Rightarrow I_4 + I_5 + I_6 &= 0 \\ \Rightarrow \frac{V_B - V_A}{5} + \frac{V_B - V_o}{5} + 1 &= 0 \\ \Rightarrow V_B - V_A + V_B + 5 &= 0 \\ \Rightarrow -V_A + 2V_B &= -5 \quad \text{--- (2)} \end{aligned}$$

Solving eq. (1) & (2)

$$V_A = 9.02 \text{ V}$$

$$V_B = 2.012 \text{ V}$$


$$I_{4\Omega} = I_2 = \frac{V_A - V_o}{4} = \frac{9.02}{4} = 2.255 \text{ A}$$

$$I_{4\Omega} = 2.55 \text{ A}$$

Thevenin's Theorem

- It is a network reduction theorem.
- It reduce the complexity of the circuit
- It simplify the circuit.
- According to the thevenin's theorem, any linear bilateral network irrespective of its complexities can be reduced into a Thevenin's equivalent circuit having the Thevenin's open circuit voltage ' V_{th} ' in series with the Thevenin's equivalent resistance ' R_{th} ' along with load resistor R_L .

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

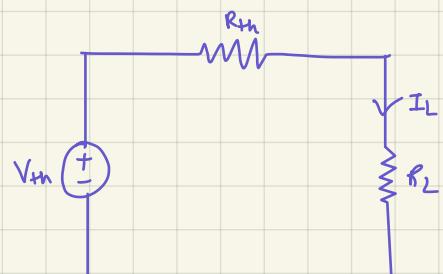

V_{th} = Thevenin voltage / open circuit voltage

R_{th} = Thevenin resistance

R_L = Load Resistance (to be calculated / to find ?)

I_L = Load Current.

Steps:-

- 1) Identify the load resistor R_L
- 2) Remove the load resistor and calculate the open circuit potential across two open ends. This will be Thevenin's equivalent voltage V_{th} .
- 3) Again remove the load resistor and replace all the active sources by their internal resistors
- 4) Calculate the equivalent resistance across the open ends. This will be the Thevenin's equivalent resistance R_{th} .
- 5) Draw the Thevenin's equivalent for given network.
- 6) Calculate the load current I_L by using the identity

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

Limitations

Thevenin's theorem cannot be applied to a network which contains non linear impedances. We cannot calculate the power consumed internally or efficiency of a circuit.

1) Draw the given circuit

2) Ground the circuit.

3) Thevenin \rightarrow Thévenin resistance.

4) Replace the Load resistance \rightarrow any voltage

Main voltage \rightarrow remove.

5)

$$\frac{V}{I} = \frac{10}{2.5926} = R_{th} = 38.57 \Rightarrow R_{th}$$


6) Make the equivalent circuit of thevening

$V_{th} \rightarrow$ 2nd circuit \rightarrow when
resistance is made high.
↓
voltage through load branch.

$$R_{th} = \frac{30V}{2.903A} = \underline{\underline{10.334}}$$

$$R_{th} = \frac{60}{1.424A} = \underline{\underline{42.134}}$$

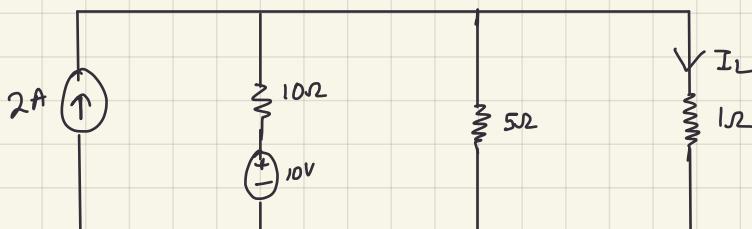Q1. Find the current through R_L resistor in the given circuit using Thévenin's theorem.



Soln - • $R_L = 1\Omega$

- Removing R_L we get $\Rightarrow 2A$
- Applying mesh analysis

For mesh ①

$$\Rightarrow I_1 = 2A$$


For mesh ②

$$\Rightarrow 10 - 10(I_2 - I_1) - 5I_2 = 0$$


$$\Rightarrow -15I_2 + 10I_1 = -10$$

$$\Rightarrow -15I_2 = -30$$

$$\Rightarrow I_2 = 2 \text{ Amp}$$

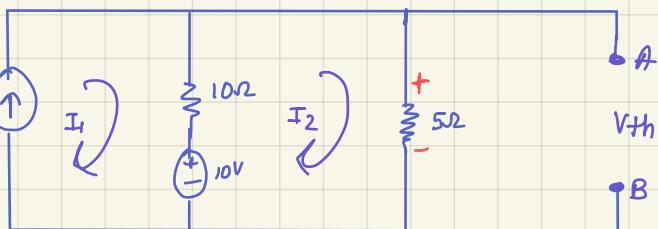

• Drawing the equivalent circuit.

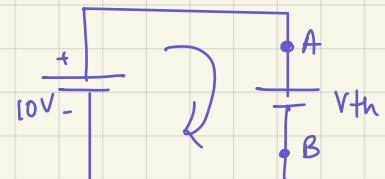


$$\Rightarrow -V_{th} + 10 = 0$$

$$\Rightarrow V_{th} = 10V$$

- Active sources will get replaced by internal sources.

\Rightarrow voltage source: 0Ω \rightarrow short circuit
(resistance)

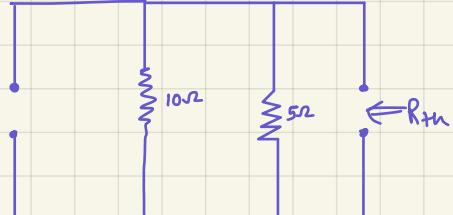\Rightarrow current source: ∞ (infinite resistance) \rightarrow open circuit



∴ Removing R_L and replacing

$$\Rightarrow 10 || 5$$

$$\Rightarrow \frac{10 \times 5}{10+5} = \frac{50}{15} = 3.33\Omega$$

$$\Rightarrow R_{th} = 3.333\Omega$$

$$R_{th} = 3.33\Omega$$



$$I_L = \frac{V_{th}}{R_{th} + R_L}$$


$$= \frac{10}{3.33 + 1} = \frac{10}{4.33} = 2.309$$

$$I_L = 2.309 \text{ Amp}$$

NORTON'S THEOREM

- It is a network reduction theorem.
- It reduce the complexity of the circuit
- It simplify the circuit.
- According to Norton's theorem, Any linear bilateral network irrespective of its complexities can be reduced into a Norton's equivalent circuit having a Norton's short circuit current 'IN' in parallel with Norton's equivalent resistance R_N in parallel with load resistor R_L .

$$I_L = \frac{I_N R_N}{R_L + R_N}$$

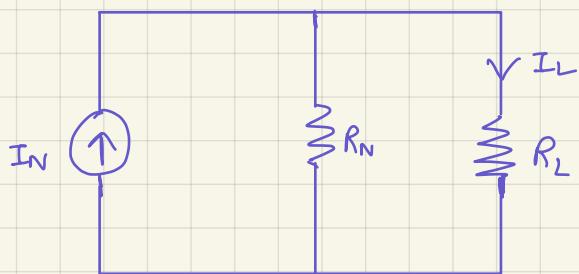

Steps:-

- 1) Identify the load resistor R_L
- 2) Replace R_L with a short circuit branch
- 3) The current flowing through this short circuit branch will be the Norton's current I_N .
- 4) Remove R_L and replace all the active sources by their internal resistance.
- 5) The equivalent resistance across the two open will be the Norton's resistance R_N
- 6) Draw the norton's equivalent circuit.
- 7) Calculate I_L using the Identity.

$$I_L = \frac{I_N R_N}{R_N + R_L}$$


$I_N \rightarrow$ norton current \rightarrow current source
 \downarrow
 $2nd$ circuit \rightarrow negligible value.

$$R_N \rightarrow \frac{20}{680.85} = \frac{\text{2nd circuit}}{\text{Calculate}}$$

(2nd last)

$$\Rightarrow \frac{60}{1.424} \quad IDC = \frac{\text{2nd circuit}}{\text{load current}}$$

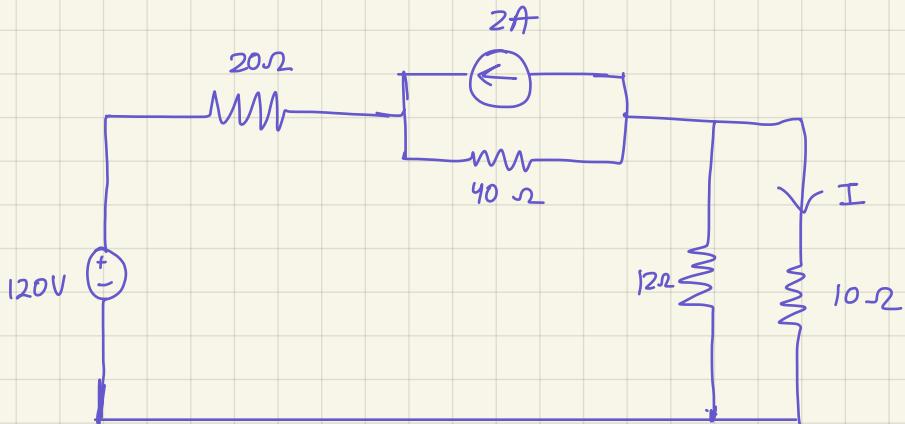Q. find the current I in the given circuit using Norton's Theorem.



$$\text{Soln: } R_L = 10\Omega$$

Replacing the load resistor with a short circuit branch

$$\text{mesh 1: } I_1 = -2A \quad \text{--- (1)}$$

$$\begin{aligned} \text{mesh 2: } & -72I_2 + 40I_1 + 12I_3 = -120 \\ & -72I_2 + 12I_3 = -40 \quad \text{--- (2)} \end{aligned}$$

$$\text{mesh 3: } -12I_3 + 12I_2 = 0 \quad \text{--- (3)}$$

Following (1)(2)(3)

$$I_1 = -2A$$

$$I_2 = 0.666 A$$




$$I_3 = 0$$

- $I_N = I_2 = 0.666 A \rightarrow \text{Norton Current}$

- Removing R_L and replacing all the active sources by their internal resistance.

- $R_N = (20+40) // 12$
 $= \frac{60 \times 12}{60+12}$

$$R_N = 10\Omega$$

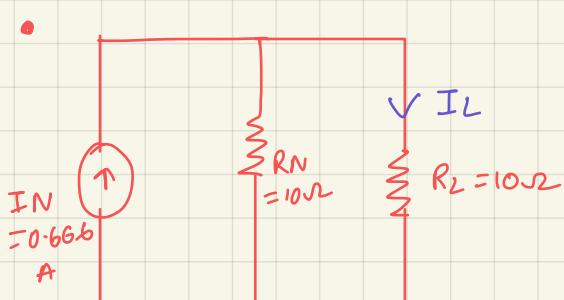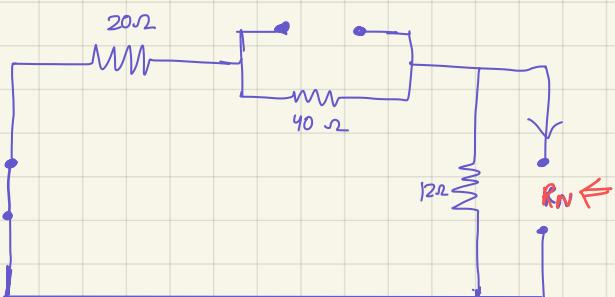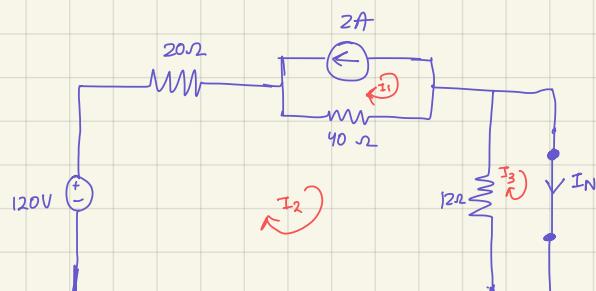

$$I_L = \frac{I_N R_N}{R_N + R_L}$$

$$= \frac{0.666 \times 10}{10 + 10}$$

$$I_L = 0.333 A$$


SUPERPOSITION THEOREM

- According to the SPT, in any linear bilateral multi source network, the current or voltage across any branch can be calculated by taking the algebraic sum of values calculated by taking one source at a time and replacing the other active sources by their internal resistances.

STEPS


- 1) Identify the branch and quantity to be calculated along with the presence of more than 1 active source.
- 2) Consider any 1 active source and replace the remaining by their internal resistances.
- 3) Calculate the required electrical quantity for that particular source.
- 4) Repeat the last 2 steps for all the active sources.
- 5) Algebraic sum of all these individual values will be the final value of required electrical quantity for all the sources working together.

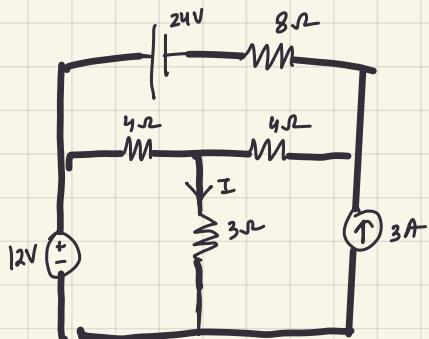Q1. For the given circuit using the super position theorem calculate I .



There are 3 active sources in the given network.

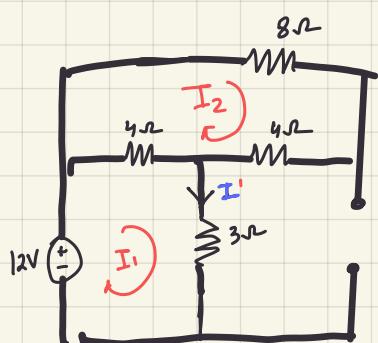- Taking 12V source and replacing all the other active sources by their internal resistances.



$$\text{Mesh 1 : } -7I_1 + 4I_2 = -12 \quad (1)$$


$$\text{Mesh 2 : } -16I_2 + 4I_1 = 0 \quad (2)$$

Solving (1) & (2)

$$\Rightarrow I_1 = 2A$$

$$\Rightarrow I_2 = 0.5A$$

$$\therefore I'_{(12V)} = 2A$$

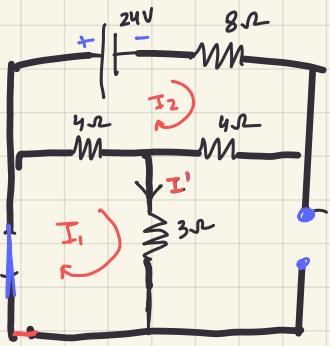

• Taking 24V source and replacing all the other active sources by their internal resistances.

$$\text{Mesh 1: } -7I_1 + 4I_2 = 0 \quad \text{--- (1)}$$


$$\text{Mesh 2: } -16I_2 + 4I_1 = 24 \quad \text{--- (2)}$$

Solving (1) & (2)

$$I_1 = -1 \text{ A}$$

$$I_2 = -1.75 \text{ A}$$

$$\therefore I'_{(24V)} = -1 \text{ A}$$

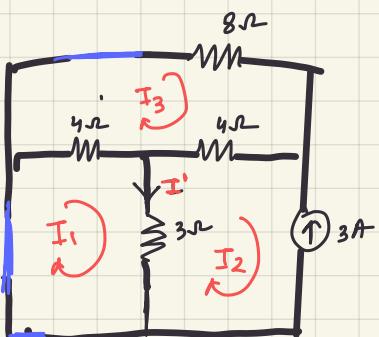

• Taking 3A source and replacing all the other active sources by their internal resistances

$$\text{Mesh 1: } -7I_1 + 3I_2 + 4I_3 = 0$$

$$\text{Mesh 3: } -4I_1 - 4I_2 - 16I_3 = 0$$

$$\text{Mesh 2: } I_2 = -3 \text{ Amp}$$

Solving
 $I_1 = -2 \text{ Amp}$
 $I_2 = -3 \text{ Amp}$
 $I_3 = -1.25 \text{ Amp}$

$$I'_{(3A)} = I_1 - I_2 = -2 - (-3) \\ = 1 \text{ amp}$$


$$I'_{(3A)} = 1 \text{ (amp)}$$

As per Superposition theorem,

$$I_T = I_{(12V)} + I_{(24V)} + I_{(3A)}$$



$$= 2 - 1 + 1$$

$$I_T = 2 \text{ Amp}$$

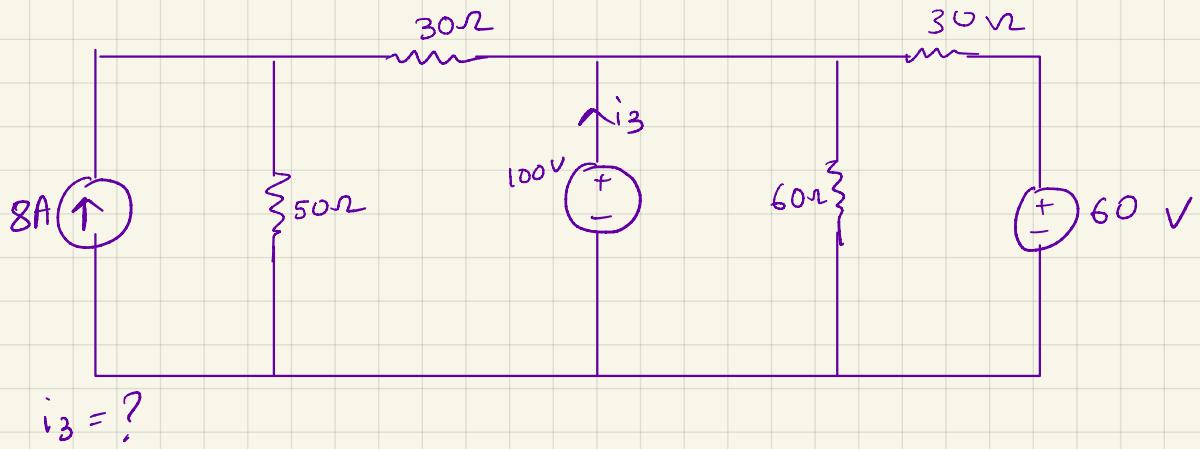


Step 1: let's assume only $8A$ current source is acting.
 \therefore other sources are deactivated

\therefore circuit \Rightarrow

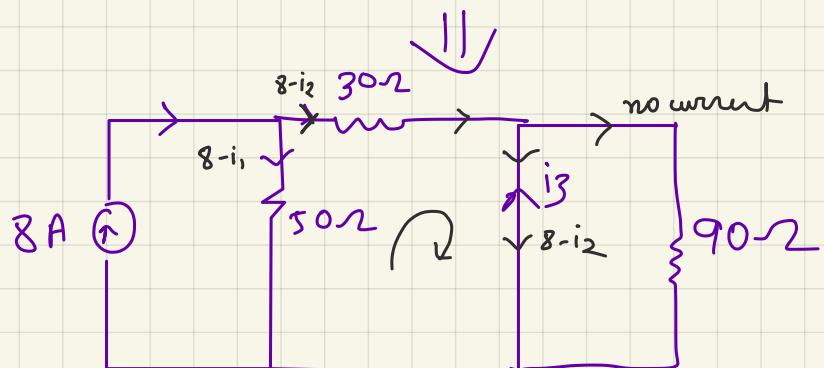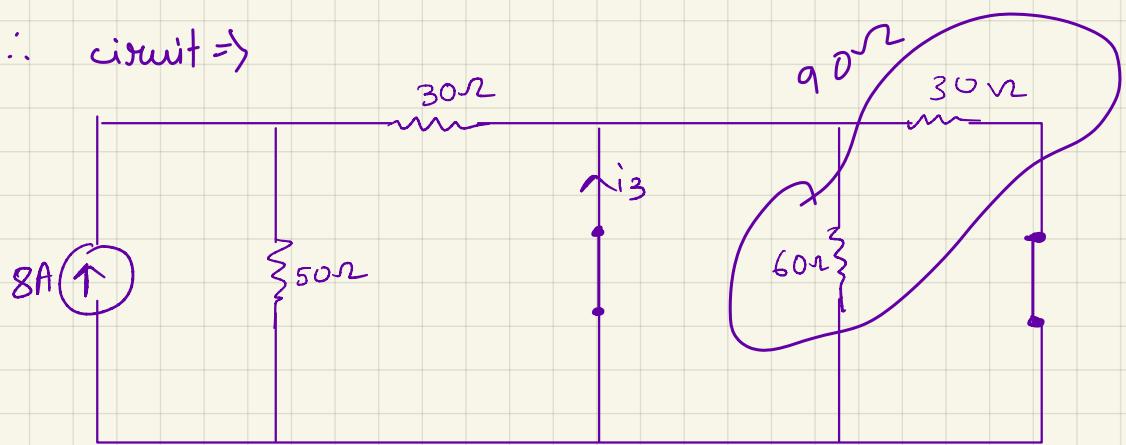

Maximum Power Transfer Theorem

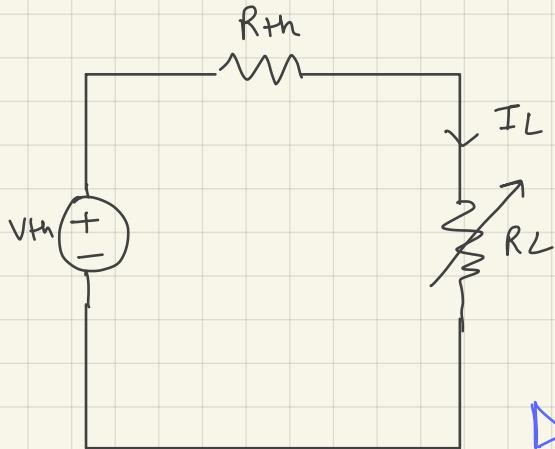According to the maximum power transfer theorem the condition for minimum power flow through load resistor R_L can be achieved when the load resistor equals to the Thvenin's equivalent resistance of the circuit.



$$\text{Power through } R_L : P = I_L^2 R_L$$

$$\bullet \quad I_L = \frac{V_{th}}{R_{th} + R_L}$$

$$\therefore P = \left(\frac{V_{th}}{R_{th} + R_L} \right)^2 R_L \quad \text{--- (2)}$$

Differentiating the above eqn with R_L and equating it to zero.

$$\frac{dP}{dR_L} = V_{th}^2 \left[\frac{(R_{th} + R_L)^2 - 2R_L(R_{th} + R_L)}{(R_{th} + R_L)^4} \right] = 0$$

$$\Rightarrow R_{th}^2 - R_L^2 = 0$$

$$\Rightarrow R_L = R_{th} \quad \text{--- (3)}$$

CONDITION
when the load resistance is equal to peak resistance then peak amount power we will get.

Now putting the value of $R_L = R_{th}$ in eq (2)


$$\therefore P_{max} = \frac{V_{th}^2}{(R_{th} + R_{th})^2} \cdot R_{th}$$

$$= \frac{V_{th}^2}{4R_{th}^2} \cdot R_{th}$$

$$P_{max.} = \frac{V_{th}^2}{4R_{th}}$$

Amount of max Power transferred.

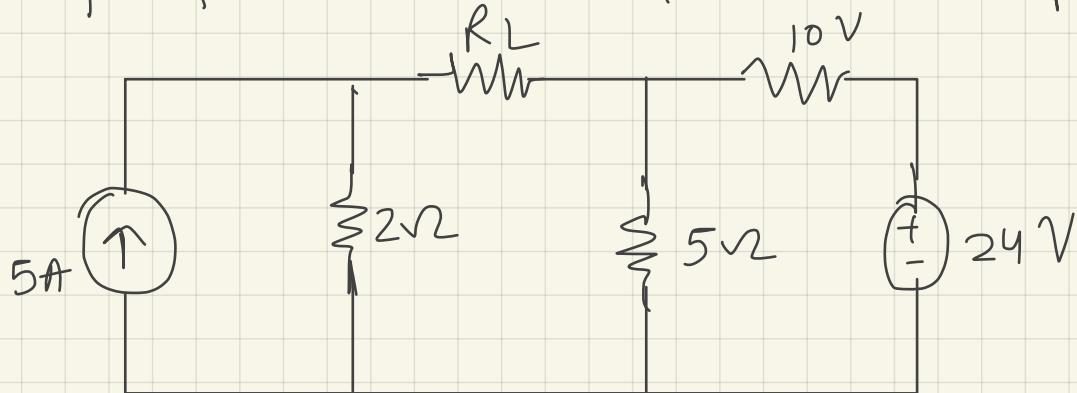Q1. In the given network find the value of R_L , which will absorb the maximum power from the source. Also find the maximum power.



R, C, L

- Resistance → Same phase

- Capacitor → Current lead by 90° (CCL) → potential lag.

$$\mathcal{E} = \mathcal{E}_0 \sin \omega t$$

$$i = \frac{\mathcal{E}_0}{\frac{1}{\omega C}} \sin(\omega t + \frac{\pi}{2})$$

→ Capacitive reactance

$$\Rightarrow X_C = \frac{1}{\omega C} \quad \Omega \rightarrow \text{unit}$$


- Inductor → Potential lead by 90° (IPL) → current lag.

$$\rightarrow \mathcal{E} = \mathcal{E}_0 \sin(\omega t)$$


$$\rightarrow i = \frac{\mathcal{E}_0}{\omega L} \sin(\omega t - \frac{\pi}{2})$$

→ Inductive reactance

$$X_L = \omega L$$

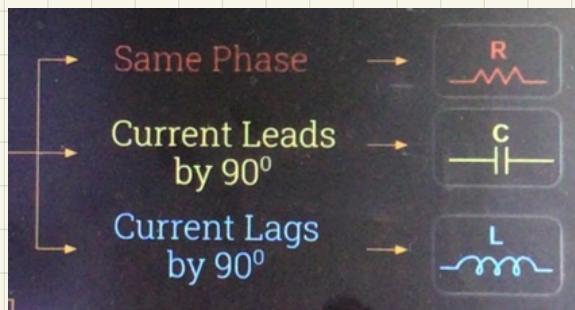

→ LCR circuit

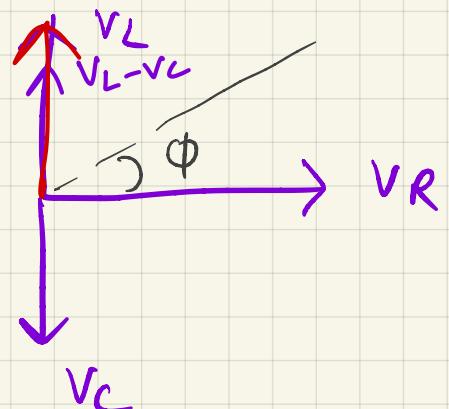

Reactance		
Resistance	Capacitor	Inductor
'R'	$X_C = \frac{1}{\omega C}$	$X_L = \omega L$
	$X_C = \frac{1}{2\pi f C}$	$X_L = 2\pi f L$
	$f = 0, X_C \rightarrow \infty$	$f = 0, X_L = 0$

$$\tan \phi = \frac{X_C - X_L}{R}$$

$$\tan \phi = \frac{V_L - V_C}{V_R}$$

- Impedance $= \sqrt{R^2 + (X_L - X_C)^2}$

\hookrightarrow min when $X_L = X_C$: when resonate.

When resonate occurs, $X_L = X_C \Rightarrow Z = R$
 then current becomes maximum.

i.e $i_0 = \frac{E_0}{\sqrt{R^2 + (X_L - X_C)^2}}$

Now, $X_L = X_C$

$$\Rightarrow \omega L = \frac{1}{\omega C}$$

$$\Rightarrow \omega = \frac{1}{\sqrt{LC}}$$

The effective resistance in an electric circuit or component of an are the combined networks of ohmic resistance and reactance is called impedance

- Power factor - Power consumed by any circuit
Denoted by $\cos \phi$.

$$\cos \phi = \frac{R}{Z} < 1$$

$$\cos \phi = \frac{\text{Resistance}}{\text{Impedance}}$$

$$\sqrt{R^2 + (X_L - X_C)^2}$$

- Quality factor - It determines the sharpness of a frequency

$$Q = \frac{\omega_0 L}{R} \rightarrow \frac{X_L}{R} \rightarrow \frac{\text{Inductance Reactance}}{\text{Resistance.}} \rightarrow \text{Dimension less.}$$

At resonance, I is maximum. Hence V_L or V_C is maximum.

$X_L = X_C \Rightarrow V_L = V_C$

Quality factor = $\frac{\text{Voltage across inductor or capacitor at resonance}}{\text{applied voltage}}$

$$Q = \frac{V_L \text{ or } V_C}{V_0} = \frac{i_0 X_L \text{ or } i_0 X_C}{i_0 R} = \frac{X_L}{R} \text{ or } \frac{X_C}{R}$$

$Q = \frac{\omega L}{R} \text{ or } \frac{1}{\omega C R}$

- In series resonance, impedance of circuit is minimum and ($Z = R$)


Current is maximum.

$$I = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}}$$

NORTON

- According to Norton's theorem, Any linear bilateral network irrespective of its complexities can be reduced into a Norton's equivalent circuit having a Norton's short circuit current 'I_N' in parallel with Norton's equivalent resistance R_N in parallel with load resistor R_L.

$$I_L = \frac{I_N R_N}{R_L + R_N}$$

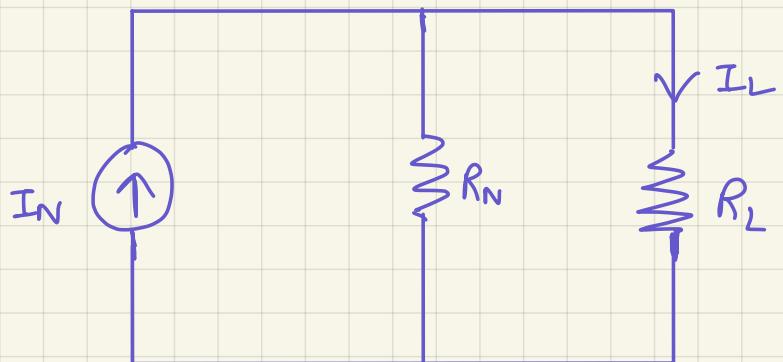

Thevening

- According to the Thevenin's theorem, any linear bilateral network irrespective of its complexities can be reduced into a Thevenin's equivalent circuit having the Thevenin's open circuit voltage 'V_{th}' in series with the Thevenin's equivalent resistance 'R_{th}' along with load resistor R_L.


$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

V_{th} = Thevenin voltage / open circuit voltage

R_{th} = Thevenin resistance

R_L = Load Resistance (to be calculated / To find ?)

I_L = Load Current.

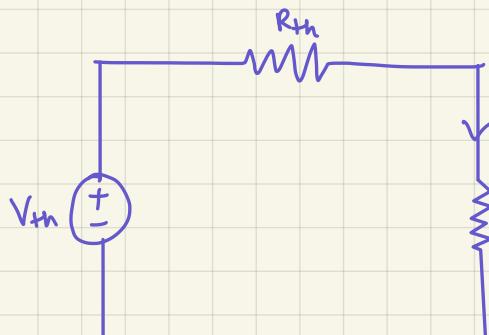


SUPERPOSITION THEOREM

- According to the SPT, in any linear bilateral multi source network, the current or voltage across any branch can be calculated by taking the algebraic sum of values calculated by taking one source at a time and replacing the other active sources by their internal resistances.

Maximum Power Transfer Theorem

According to the maximum power transfer theorem the condition for minimum power flow through load resistor R_L can be achieved when the load resistor equals to the Thvenins' equivalent resistance of the circuit.

● Shunt Generator Diagram

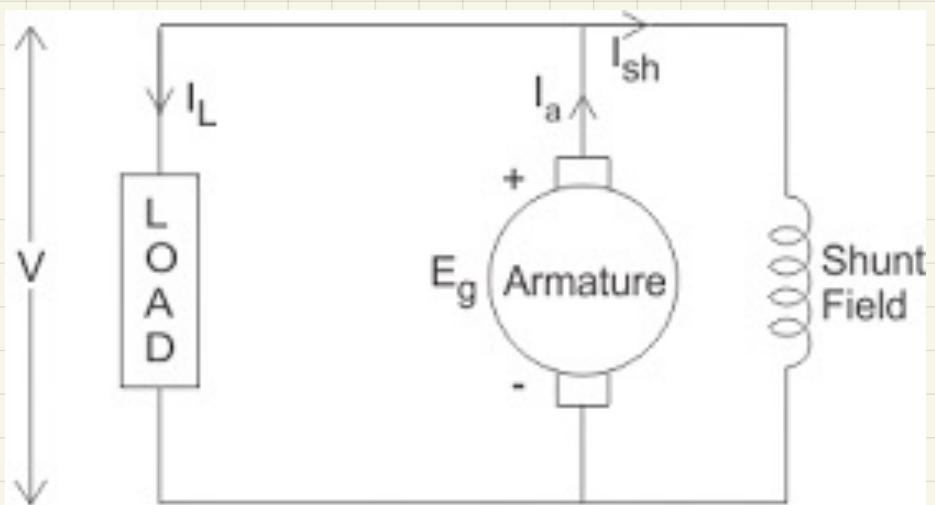

Shunt Wound Generator



Why do you replace voltage sources with short circuits and current sources with open circuits in Thevenin's and Norton's theorem?

→ Voltage → Zero → value is made zero to convert it Impedance into IDEAL voltage source
 ↗?

An ideal voltage source can produce whatever current it needs to keep its terminal voltage at specified value.

→ Current → zero → To make it ideal → ideal source has INFNITE Impedance which is open circuit

↗ Why?

↗ It can produce whatever voltage needs to flow through the specified current.

- unit of active power — ampere
- Active power — true power perform the real work

$$P \rightarrow I^2 R$$

$$P = V I$$

$$P = (V_0 \sin \omega t) I$$

$$\bullet \text{Form Factor} = \frac{I_{\text{rms}}}{I_{\text{av}}} = \frac{\underline{I \cdot I}}{\underline{I_{\text{av}}}} = \frac{V_{\text{rms}}}{V_{\text{average}}}$$

$$\bullet \text{Peak Factor} = \frac{I_m}{I_{\text{rms}}} = \frac{E_m}{E_{\text{rms}}}$$

$$\bullet \text{India} \rightarrow 50 \text{ Hz} \rightarrow \underline{\underline{230 \text{ V}}}$$

AVERAGE VALUE OF Current/Voltage

In Full Cycle or Long Period

$$\langle I \rangle = I_{\text{avg}} = I_{\text{mean}} = \bar{I} = \frac{\int_0^T I dt}{\int_0^T dt} = 0$$

In Half Cycle

$$I_{\text{avg}} = I_{\text{mean}} = \bar{I} = \frac{\int_0^{T/2} I dt}{\int_0^{T/2} dt} = \frac{2I_0}{\pi} = 0.637I_0$$



$$I_{\text{av}} = \frac{2I_0}{\pi} = 0.637I_0$$

$$V_{AV} = \frac{2V_0}{\pi} = 0.637V_0$$

RMS - It is the root of average value of I^2 over a time period.

$$I_{\text{rms}} = \sqrt{\frac{\int_0^T I^2 dt}{\int_0^T dt}}$$


$\frac{1}{2}$ cycle : $I_{\text{rms}} = \frac{I_0}{\sqrt{2}} = 0.707I_0$

$\therefore I_{\text{rms}} = \frac{\text{Peak } I}{\sqrt{2}}$

Rms Value of Current

R.M.S. Root Mean Squared Value

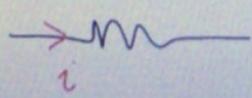The R.m.s. value or Virtual value or Effective value of any current is defined as that value of steady (constant) current which would generate the same amount of heat in a given resistance in a given time as generated by actual current passing through the same resistance for the same given time.



$$H = \int_{t_1}^{t_2} i^2 R dt$$

$$H = \int_{t_1}^{t_2} i(t)^2 R dt$$

$$i_{\text{rms}}^2 R t = \int_{t_1}^{t_2} i(t)^2 R dt$$

unacademy


Similarly, rms value of emf is

$$E_{\text{rms}} = \frac{E_0}{\sqrt{2}} = 0.707 E_0$$

Where E_0 is maximum emf

In Full Cycle	$V_{\text{avg}} = V_{\text{mean}} = \bar{V} = \frac{\int_0^T V dt}{\int_0^T dt} = 0$
In Half Cycle	$V_{\text{avg}} = V_{\text{mean}} = \bar{V} = \frac{\int_0^{T/2} V dt}{\int_0^{T/2} dt} = \frac{2V_0}{\pi} = 0.637V_0$
In Full / Half Cycle	$V_{\text{rms}} = V_{\text{effective}} = \sqrt{\bar{V}^2} = \frac{V_0}{\sqrt{2}} = 0.707V_0$
In long period of time	$V_{\text{rms}} = \frac{V_0}{\sqrt{2}} = 0.707V_0 \quad V_{\text{mean}} = V_{\text{avg}} = 0$ 

Only resistive \Rightarrow same phase

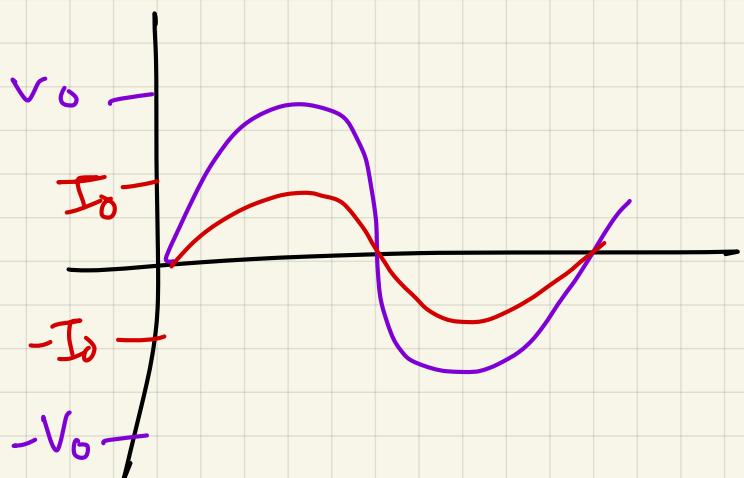


$$i_0 = \frac{\epsilon_0}{R}$$

$$i = \frac{\epsilon}{R}$$

$$\epsilon = \epsilon_0 \sin \omega t$$

$$i = i_0 \sin \omega t$$

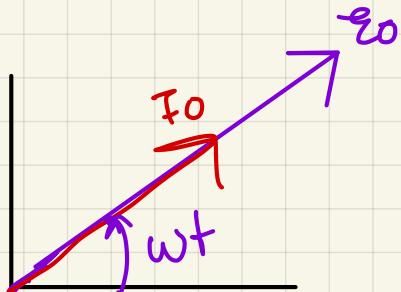

Only Inductive IPL

$$V_L = L \frac{di}{dt}$$

$$I = I_0 \sin\left(\omega t - \frac{\pi}{2}\right)$$

$$DC \Rightarrow \omega = 0$$

$$XL = 0$$

inductor offer zero resistance
to DC

A transformer may be defined as a static electric device that transfers electrical energy from one circuit to another circuit at the same frequency but with changed voltage (or current or both) through a magnetic circuit.

EMF Equation:

$$e = -Nd\phi/dt$$

$$e = -2\pi f \phi_{max} N_{ws} \text{ wt V}$$

$$E_{max} = 2\pi f \phi_{max} N V$$

$$E_{rms} = 4.44 \phi_{max} f N V$$

RMS value of voltage induced at primary,

$$E_1 = 4.44 \phi_{max} f N_1 V$$

RMS value of voltage induced at secondary,

$$E_2 = 4.44 \phi_{max} f N_2 V$$

Type of Transformer (single phase)

i) Core type - Pg. 532

ii) Shell type - Pg. 532

* Lamination reduce eddy current loss

* Silicon steel reduces hysteresis loss.

• Transformation Ratio $\Rightarrow \frac{E_1}{E_2} = \frac{N_1}{N_2}$ (Pg - 533)

The ratio of primary voltage to secondary voltage is same as the ratio of primary winding turns to the secondary winding turns.

When $N_1 > N_2$ then $E_2 < E_1$
Step up transformer.

2) When $N_2 > N_1$ then $E_2 > E_1$
then it's step down transformer

• Impedance Transformer

- impedance Z_2 is connected across the secondary winding at its output.

Pg - 534

12 Transformer

12 - 12:20 3phase

12 : 20 - 30 AC
RLC

30 - 40 - DC
Network


40 - 50 Viva
Questions

NORTON'S THEOREM

- It is a network reduction theorem.
 - It reduce the complexity of the circuit
 - It simplify the circuit.

— According to Norton's theorem, Any linear bilateral network irrespective of its complexities can be reduced into a Norton's equivalent circuit having a Norton's short circuit current ' I_N ' in parallel with Norton's equivalent resistance R_N in parallel with load resistor R_L .

$$I_L = \frac{I_N R_N}{R_L + R_N}$$

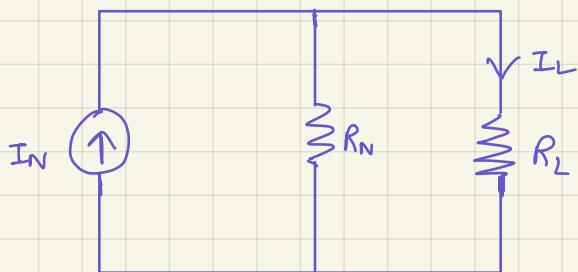

Steps :-

- 1) Identify the load resistor R_L
 - 2) Replace R_L with a short circuit branch
 - 3) The current flowing through this short circuit branch will be the Norton's current I_N .
 - 4) Remove R_L and replace all the active sources by their internal resistance
 - 5) The equivalent resistance across the two open will be the Norton's resistance R_N
 - > Draw the norton's equivalent circuit.

Calculate I_L using the Identity.

$$I_L = \frac{I_N R_N}{R_N + R_L}$$

\rightarrow Norton current \rightarrow current source
 \rightarrow 2nd circuit \rightarrow negligible rate.


$$R_N \rightarrow \frac{20}{680.85} = \frac{\text{Find circuit}}{\text{Calculate}} \quad (2nd \text{ last})$$

$$\Rightarrow \frac{60}{1.424} \quad IDC = \boxed{\text{2nd circuit load current}}$$

Thevenin's Theorem

- It is a network reduction theorem.
- It reduce the complexity of the circuit
- It simplify the circuit.
- According to the thevenin's theorem, any linear bilateral network irrespective of its complexities can be reduced into a Thevenin's equivalent circuit having the Thevenin's open circuit voltage ' V_{th} ' in series with the Thevenin's equivalent resistance ' R_{th} ' along with load resistor R_L .

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

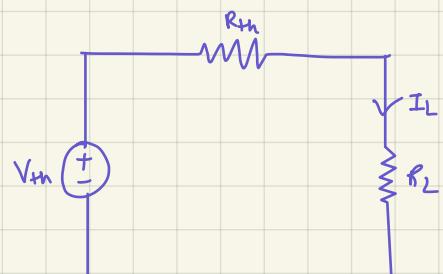

V_{th} = Thevenin voltage / open circuit voltage

R_{th} = Thevenin resistance

R_L = Load Resistance (to be calculated / to find ?)

I_L = Load Current.

Steps:-

- 1) Identify the load resistor R_L
- 2) Remove the load resistor and calculate the open circuit potential across two open ends. This will be Thevenin's equivalent voltage V_{th} .
- 3) Again remove the load resistor and replace all the active sources by their internal resistors
- 4) Calculate the equivalent resistance across the open ends. This will be the Thevenin's equivalent resistance R_{th} .
- 5) Draw the Thevenin's equivalent for given network.
- 6) Calculate the load current I_L by using the identity

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

Limitations

Thevenin's theorem cannot be applied to a network which contains non linear impedances. It cannot calculate the power consumed internally or efficiency of a circuit.

Rectifier — A rectifier is a device that converts an oscillating two-directional alternating current (AC) into a single-directional direct current (DC)

A full wave same as half wave, but it allows unidirectional current through the load during the sinusoidal cycle.

Inverter — while an inverter converts DC to AC.

Diode — A diode is defined as a two-terminal electronic component that only conducts current in one direction

Transformer — Definition

A transformer is a passive electrical device that transfers electrical energy from one electrical circuit to another, or multiple circuits.

Zener diode is a special type of diode designed to reliably allow current to flow "backwards" when a certain set reverse voltage, known as the Zener voltage

Uses

A transformer is an electrical apparatus designed to convert alternating current from one voltage to another. It can be designed to "step up" or "step down" voltages and works on the magnetic induction principle.

Filter

↳ A filter is a circuit capable of passing / amplifying certain frequencies while attenuating other frequencies.

4.2 CHARACTERISTICS OF NETWORK ELEMENTS

4.2.1 Linear and Non-linear Elements

A *linear element* shows linear characteristics of voltage vs current. Thus the parameters of linear elements remain constant (i.e., the parameters do not change with voltage or current applied to that element). Resistors, inductors and capacitors are linear elements.

On the other hand, for a *non-linear element*, the current passing through it does not change linearly with the linear change in applied voltage across it, at a particular temperature and frequency. In a non-linear element the parameters change with applied voltage and current changes. Semiconductor devices like diodes, transistors, thyristors, etc. are typical examples of non-linear elements. Ohm's law is not valid for non-linear elements.

*A network element is a component of a circuit having different characteristics like linear, non-linear, active or passive etc. and will be defined shortly.

Difference between full wave & half wave

Full-wave rectification rectifies the negative component of the input voltage to a positive voltage, then converts it into DC (pulse current) utilizing a diode bridge configuration.

In contrast, half-wave rectification removes just the negative voltage component using a single diode before converting to DC.

Afterward, the waveform is smoothed by charging/discharging a capacitor, resulting in a clean DC signal.

Bridge Rectifier

We can define bridge rectifiers as a type of full-wave rectifier that uses four or more diodes in a bridge circuit configuration to efficiently convert alternating (AC) current to a direct (DC) current.

Copper loss is the term often given to heat produced by electrical currents in the conductors of **transformer** windings, or other electrical devices. which result from induced currents in adjacent components.

Lower current is passed at a higher voltage across the wires.

2. Thicker wires are used to reduce resistance (R) as R is inversely proportional to area of cross section of wire.

When the flux links with a closed circuit, an emf is induced in the circuit and the current flows, the value of the current depends upon the amount of emf around the circuit and the resistance of the circuit.

The eddy current loss is minimized by making the core with thin laminations.

Iron losses are caused by the alternating flux in the core of the transformer as this loss occurs in the core it is also known as Core loss. Iron loss is further divided into hysteresis and eddy current loss.

The iron or core losses can be minimized by using silicon steel material for the construction of the core of the transformer

The core of the transformer is subjected to an alternating magnetizing force, and for each cycle of emf, a hysteresis loop is traced out. Power is dissipated in the form of heat known as hysteresis loss

Stray Loss

The occurrence of these stray losses is due to the presence of leakage field. The percentage of these losses are very small as compared to the iron and copper losses so they can be neglected.

Dielectric Loss

Dielectric loss occurs in the insulating material of the transformer that is in the oil of the transformer, or in the solid insulations. When the oil gets deteriorated or the solid insulation gets damaged, or its quality decreases, and because of this, the efficiency of the transformer gets affected.

What is Active Power: (P)

Active Power is the actual power which is really transferred to the load such as **transformer**, induction motors, generators etc and dissipated in the circuit.

The unit of Real or Active power is Watt where $1W = 1V \times 1A$.

What is Reactive Power: (Q)

Also known as **(Use-less Power, Watt less Power)**

The powers that continuously bounce back and forth between source and load is known as reactive Power (Q)

The unit of **Reactive Power** is Volt-Ampere reactive i.e. **VAR** where $1 VAR = 1V \times 1A$.

Star connection

$$V_L = \sqrt{3} V_{ph}$$

$$I_L = I_{ph}$$

$$\text{Power} = \sqrt{3} I_L V_L \cos\theta$$

Delta connection

$$V_L = V_{ph}$$

$$I_L = \sqrt{3} I_{ph}$$

Power

What is Apparent Power: (S)

The **Product of voltage and current if and only if the phase angle differences between current and voltage are ignored**

The unit of Apparent power (S) VA i.e. $1VA = 1V \times 1A$.

What is Complex Power ?

($S = P+jQ$ or $S=VI^*$)

The Complex sum of **Real Power (P)** and **Reactive Power (Q)** is known as **Complex Power** which can be expressed like $S = P+jQ$ and measured in terms of **Volt Amps Reactive** (generally in kVAR)

What is Power Factor?

Power factor may be defined by three definitions and formulas as follow.

You may also read: [Is Reactive Power Useful?](#)

1). The Cosine of angle between Current and Voltage is called Power Factor.

$$P = VI \cos\theta \text{ OR}$$

$$\cos\theta = P / VI \text{ OR}$$

$$\cos\theta = kW / kVA \text{ OR}$$

$$\cos\theta = \text{True Power/ Apparent Power}$$

Where:

P = Power in Watts

V = Voltages in Volts

I = Current in Amperes

W = Real Power in Watts

VA = Apparent Power in Volt-Amperes or kVA

Cosθ = Power factor

2). The ratio between Resistance and Impedance in AC Circuit is known

$$\cos\theta = R/Z$$

Where:

R = Resistance in Ohms (Ω)

Z = Impedance (Resistance in AC circuits i.e. X_L , X_C and R known as **Inductive reactance, capacitive reactance and resistance** respectively) in Ohms (Ω)

Cosθ = Power factor

Impedance "Z" is the total resistance of AC Circuit i.e.

$$Z = \sqrt{[R^2 + (X_L + X_C)^2]}$$

Where:

$$X_L = 2\pi f L \quad \dots \text{L is inductance in Henry}$$

$$X_C = 1 / 2\pi f C \quad \dots \text{C is capacitance in Farads}$$

Related Post: [Difference Between Active and Reactive Power](#)

3). The ratio between Active Power and Apparent Power in volts-amperes is called power factor.

$$\cos\theta = \text{Active Power / Apparent Power}$$

$$\cos\theta = P / S$$

$$\cos\theta = kW / kVA$$

Where

kW = P = Real Power in kilo-Watts

kVA = S = Apparent Power in kilo-Volt-Amperes or Watts

Cosθ = Power factor

Power Factor Formula in Three Phase AC Circuits

$$\text{Power Factor } \cos\theta = P / \sqrt{3} V_L \times I_L \quad \dots \text{Line Current & Voltage}$$

$$\text{Power Factor } \cos\theta = P / \sqrt{3} V_P \times I_P \quad \dots \text{Phase Current & Voltage}$$

In **pure resistive circuit**, power factor is 1 due to zero phase angle difference (Φ) between current and voltage.

In **pure capacitive circuit**, power factor is leading due to the lagging VARs. i.e. Voltage is lagging 90° behind the current. In other words, Current is leading 90° from voltage (Current and voltage are 90° out of phase with each others, where current is leading and voltage is lagging).

In **pure inductive circuit**, power factor is lagging due to the leading VARs i.e. Voltage is leading 90° from current. In other words, Current is lagging 90° behind the voltage (Current and voltage are 90° out of phase with each others where voltage is leading and current is lagging).

battery, transformer
semiconductor

4.2.2 Active and Passive Elements

If a circuit element has the capability of enhancing the energy level of an electric signal passing through it, it is called an active element, viz., a battery, a transformer, semiconductor devices, etc. Otherwise the element that simply allows the passage of the signal through it without enhancement is called passive element (viz., resistors, inductors, thermistors and capacitors). Passive elements do not have any intrinsic property of boosting an electric signal.

4.2.3 Unilateral and Bilateral Elements

If the magnitude of the current passing through an element is affected due to change in polarity of the applied voltage, the element is called a unilateral element. On the other hand if the current magnitude remains the same even if the polarity of the applied voltage is reversed, it is called a bilateral element. Unilateral elements offer varying impedances with variation in the magnitude or direction of flow of the current while bilateral elements offer same impedance irrespective of the magnitude or direction of flow of current. A resistor, an inductance and a capacitor, all are bilateral elements while diodes, transistors, etc. are unilateral elements.

4.10.2 Independent and Dependent Sources

The voltage or current sources which do not depend on any other quantity in the circuit (i.e. the strength of voltage or current in the sources), and do not change for any change in the connected network, are called independent sources. Independent sources are represented by circles. An independent voltage source and an independent current source is shown in Fig. 4.74.1(a) and 4.74.1(b)

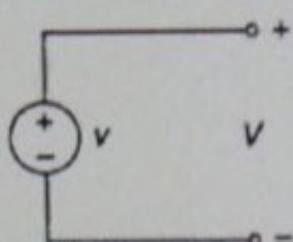


Fig. 4.74-1(a) Independent voltage source

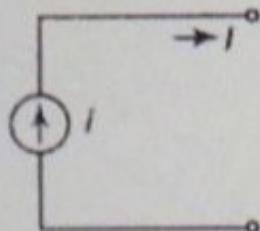


Fig. 4.74-1(b) Independent current source

A dependent voltage or current source is one which depends on some other quantity in the circuit (may be either voltage or current) i.e. the strength of voltage or current changes in the source for any change in the connected network. Dependent sources are represented by diamond-shaped symbol. There are four possible dependent sources.

R, C, L

- Resistance → Same phase

- Capacitor → Current leads by 90° (CCL) → potential lag.
- $$\mathcal{E} = \mathcal{E}_0 \sin \omega t$$

$$i = \frac{\mathcal{E}_0}{\frac{1}{\omega C}} \sin(\omega t + \frac{\pi}{2})$$

→ Capacitive reactance

$$\Rightarrow X_C = \frac{1}{\omega C} \quad \Omega \rightarrow \text{unit}$$


- Inductor → Potential lead by 90° (IPL) → current lag.

$$\rightarrow \mathcal{E} = \mathcal{E}_0 \sin(\omega t)$$


$$\rightarrow i = \frac{\mathcal{E}_0}{\omega L} \sin(\omega t - \frac{\pi}{2})$$

→ Inductive reactance

$$X_L = \omega L$$

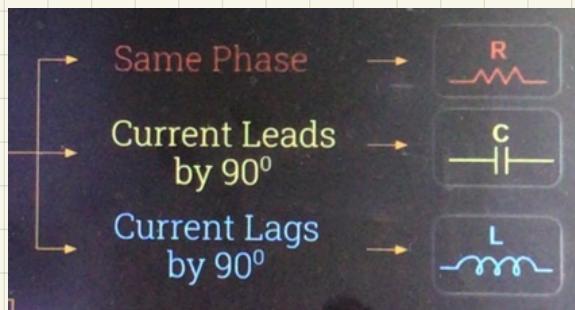

→ LCR circuit

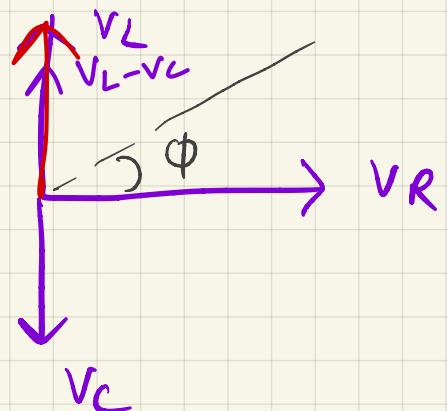

Reactance		
Resistance	Capacitor	Inductor
'R'	$X_C = \frac{1}{\omega C}$	$X_L = \omega L$
	$X_C = \frac{1}{2\pi f C}$	$X_L = 2\pi f L$
	$f = 0, X_C \rightarrow \infty$	$f = 0, X_L = 0$

$$\tan \phi = \frac{X_C - X_L}{R}$$

$$\tan \phi = \frac{V_L - V_C}{V_R}$$

- Impedance $= \sqrt{R^2 + (X_L - X_C)^2}$

\hookrightarrow min when $X_L = X_C$: when resonate.

When resonate occurs, $X_L = X_C \Rightarrow Z = R$
 then current becomes maximum.

i.e $i_0 = \frac{E_0}{\sqrt{R^2 + (X_L - X_C)^2}}$

Now, $X_L = X_C$

$$\Rightarrow \omega L = \frac{1}{\omega C}$$

$$\Rightarrow \omega = \frac{1}{\sqrt{LC}}$$

The effective resistance in an electric circuit or component of an are the combined networks of ohmic resistance and reactance is called impedance